		Exam.	B	ack	
	TRIBHUVAN UNIVERSITY	Level	BE	Full Marks	80
E	Examination Control Division	Programme	BEL, BEX, BEI, BCT, BAM, BIE, BAG, BAS, BCH	Pass Marks	32
	2070 Raishakh	Year / Part	I/I .	Time	3 hrs.

# Subject: - Basic Electrical Engineering (EE 401)

Candidates are required to give their answers in their own words as far as practicable. 1

- Attempt All questions. ~
- The figures in the margin indicate Full Marks. ~
- ✓ Assume suitable data if necessary.
- 1. a) State and explain Krichof's current and voltage laws. Find the current flowing through 2 ohm resistor using KCL equations.



b) Find voltage across the given load resistance  $R_L$ .



2. a) Find the current supplied by 10V source using Nodal Analysis in the circuit shown in figure below.



b) State and verify Reciprocity Theorem with an example.

[6]

[10]

[8]

[8]

- 3. a) Explain the parallel connection of inductors with suitable example and also find the equivalent inductance of the circuit.
  - b) A full wave rectified sinusoidal voltage shown in figure below. Find the average and effective value of the voltage.



4. For the circuit shown below. Calculate

- (i) Overall impedance of the circuit
- (ii) Total current taken from supply and overall power factor of the circuit
- (iii)Currents in each parallel branch
- (iv) Active, reactive and apparent power
- (v) Construct Phasor diagram for given circuit



- 5. a) Discuss the advantages of three phase system over single phase system. Mention the causes of low power factor and its measures to improve.
  - b) A 380 V, 3- $\Phi$  voltage is applied to a balanced star connected 3- $\Phi$  load of phase impedance  $(5+j9)\Omega$ . If wattmeters are connected taking Y phase reference, calculate wattmeter readings and also reactive power, apparent power and active power consumed. Take RYB phase sequence.

[10]

[6]

[8]

[8]

[16]









- b) A single phase inductive load of 4kW at a power factor of 70% (lagging) is connected across 240V, 50Hz supply. Calculate the kVAR capacity of the capacitor bank and value of capacitance that must be installed in parallel with load to bring the overall power factor to (i) unity, (ii) 85% lagging.
- 4. In the network shown in figure below, determine:
  - (i) Total impedance
  - (ii) Total current drawn from source
  - (iii)The overall power factor
  - (iv) Total Volt Amperes, Active Power and Reactive Power
  - (v) Is the circuit capacitive or inductive?
  - (vi)Construct the phasor diagram for given circuit.



5. a) The star-connected load having impedance of (12-j16)Ω per phase fed from a 50Hz three-phase, 400V, balanced supply, with the phase sequence as R-Y-B. Find the line current, power factor, active power, reactive power, reactive VA and total volt-amperes (VA).

b) Describe the measurement of 3-phase power by two wattmeter method.

\*\*\*

[6]

[8]

[8]

[16]















		-		
15 TRIBHUVAN UNIVERSITY	Exam.	В	ack	
INSTITUTE OF ENGINEERING	Level	BE	<b>Full Marks</b>	80
<b>Examination Control Division</b>	Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
2075 Ashwin	Year / Part	I/I	Time	3 hrs.

Subject: - Basic Electrical Engineering (EE401)

- $\checkmark$  Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt <u>All</u> questions.

The figures in the margin indicate <u>Full Marks</u>.

✓ Assume suitable data if necessary.

- 1. a) Differentiate between Practical Voltage Source and Practical Current Source.
  - b) The field winding of dc motor takes 1.15 A current at 20°C. If current falls to 0.26 A after working for some hours, supply voltage remaining constant, find the final working temperature of field winding. Given,  $\alpha_0 = \frac{1}{234.5}$  and voltage = 230V.
  - c) Three lapms of rating 220 V and 150 watt, 200 watt and 450 watt are connected across 200 V supply. Calculate the resistance of each lamp and the power consumed by each lamp at 200 V.
- 2. a) Solve the given network with mesh analysis to find voltage drop on 5  $\Omega$  resistors.



b) Use nodal analysis to find the current through  $4\Omega$  resistor for the network shown below.



c) State and explain superposition theorem with suitable example.

[4]

[6]

[4]

[6]

[6]

[6]

3. a) Using the venin's theorem find the current through the  $4\Omega$  for the network shown below.



E. FORE

b) Determine the power dissipated in the  $8\Omega$  resistor of the given network using stardelta and delta-star transformation.



c) How mutual inductance between two coils depends upon dimensions of core and coils. [4]

4. a). Find the form factor and peak factor of the current waveform given below.



- b) A coil of inductance 318.3 mH is connected in series with a 200Ω resistor to a 240 V,
   50 Hz supply. Calculate the current flowing, power factor, active and reactive power of the circuit. Also draw the phasor diagram.
- c)  $Z_1 = (40 j318.31)$  and  $Z_2 = (50 + j62.83)$  are connected in parallel to each other and a source of 100v, 50 Hz is applied across the overall circuit. Calculate (i) circuit current (ii) Active, reactive and apparent power.

[6]

[6]

[4]

[6]

[6]

- 5. a) Discuss the effect of low power factor. A single phase load of 7Kw operates at a power factor 0.7 lagging. It is proposed to improve the power factor to 0.9 lagging by connecting a capacitor the load. Calculate the KVAr rating of the capacitor. [3+5]
  - b) For the following unbalanced system with balanced three phase supply of 400 V, 50 Hz, calculate:

[8]

i) The line currents and neutral current

W 3.

- ii) Active and reactive power abosrbed by the circuit
- iii) Draw the phasor diagram.





P.T.C

3. a) Using Nodal analysis, determine currents in each branch of the network shown in below figure. Also find the total power loss in the network.



b) Find the value of Resistance 'R' to have maximum power transfer in the circuit as shown in below figure. Also obtain the amount of maximum power.



- 4. a) Two inductances L<sub>1</sub> and L<sub>2</sub> are connected in parallel. Derive the relation showing the equivalent inductance of the combination when mutual flux helps the individual flux. what will be the equivalent inductance of the combination when mutual flux opposes the individual flux?
  - b) Two alternating currents represented by the equations  $i_1 = 7$ sinwt and  $i_2 = 10 \sin\left(\omega t + \frac{\pi}{2}\right)$  are fed into a common conductor. Find the equation for the resultant current and its RMS value.

c) Below Figure shows a series parallel circuit. Find:

(i) total impedance

(ii) current drawn from the circuit

(iii)voltage across the parallel branches

(iv)current flowing through each parallel branch

(v) power factor

(vi)Active, reactive and apparent power

Also, draw the phasor diagram of the circuit.



200V, 50 Hz

[8]

[8]

[4]

[4]

[8]

- 5. a) A fluorescent lamp takes a current of 0.75A when connected across a 240V, 50Hz a.c supply. The power consumed by the lamp is 80 watt. Calculate the value of the capacitance to be connected in parallel with the lamp to improve the power factor to (i) unity (ii) 0.95 lagging.
  - b) The following balanced three phase loads are connected to a 415 V, three phase, four wire supply.

(i) 160 kVA at 0.7 power factor lagging
(ii) 50 kVA at 0.65 power factor leading
(iii) 50 kW at unity power factor

Calculate (a) the total load in kVA (b) the line current (c) the combined power factor

c) Prove that sum of the readings of two wattmeters is equal to the total three phase power in measurement of power of 3-phase circuit by 2 wattmeter method.

\*\*\*

[6]

[6]

[4]

15 TRIBHUVAN UNIVERSITY	Exam.	Kegi	ılar .	1
<b>INSTITUTE OF ENGINEERING</b>	Level	BE	<b>Full Marks</b>	80
<b>Examination Control Division</b>	Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
2074 Chaitra	Year / Part	I/I	Time	3 hrs.

## Subject: - Basic Electrical Engineering (EE401)

 $\checkmark$  Candidates are required to give their answers in their own words as far as practicable.

✓ Attempt <u>All</u> questions.

✓ The figures in the margin indicate Full Marks.

✓ Assume suitable data if necessary.

1. a) What is source transformation? Explain with the help of an example.

[4]

[6]

[6]

- b) A coil of stranded copper wire having a resistance of  $12\Omega$  at 25°C is embedded in the core of a large transformer supplied at 230 V. After the transformer has been in service for several hours, the resistance of the coil is found to be 13.4  $\Omega$ . What is the temperature of the core? Also find the power rating of the resistance. Assume temperature coefficient of wire as 0.00125/°C at 15°C.
- c) Find  $V_{xy}$  in the following circuit diagram.



2. a) Use loop current method to calculate the current through the  $2\Omega$  resistance for the network shown below.



b) Solve the given network with nodal analysis to find voltage drop on  $8\Omega$  resistor.



c) State and explain Norton's theorem with suitable example.

OT.A

[6]

[6]

[4]

3. a) Find power dissipated in 3  $\Omega$  resistor using Norton's theorem.



b) Calculate the value of 'R' such that maximum power will be absorbed by it in the given circuit.



- c) What is inductance? Derive the expression for two inductances in series, with mutual flux aiding each other.
- 4. a) Calculate the average (half period) value and rms value of the waveform shown below.



- b) An alternating source of emf v =200sin (314t) volts is applied to a practical coil with resistance  $20\Omega$  and inductance 0.1 H respectively. Determine (i) expression for instantaneous current and power factor (ii) active reactive and apparent power of circuit (iii) voltage drop on resistor and inductor and (iv) construct phasor diagram for above circuit.
- c) Find current flowing in each branches of the following circuit:

13



[6]

[6]

[4]

[4]

[6]

[6]

5. a) A 400V, 50 H3, 3 phase induction motor takes 60 KW power from supply mains at 0.8 power factor lagging. Calculate the capacitance per phase and KVAR rating per phase of capacitor in order to improve the power factor to 0.9 lagging using (i) star connected capacitor bank and (ii) Delta connected capacitor bank.

祭

ES.

b) Define phase order and explain its significance. A three phase balanced star connected load with (6+j8) ohm per phase is supplied by 400V, 50 HZ three phase source. Find the line and phase currents and the total power dissipated in the load.

\*\*\*

.

[8]

[2+6]

25 TRIBHUVAN UNIVERSITY	Exam.	New Back (20	66 & Later B	atch)
INSTITUTE OF ENGINEERING	Level	BE	Full Marks	80
Examination Control Division	Programme	BEL, BEX, BCT, BAME, BIE, B. Agri.	Pass Marks	32
2073 Shrawan	Year / Part	I/I	Time	3 hrs.

#### Subject: - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt <u>All</u> questions.
- ✓ The figures in the margin indicate Full Marks.
- ✓ Assume suitable data if necessary.
- 1. a) A coil has a resistance of 100 ohms, when the temperature is 20°C and 110 ohms when the temperature is 45° C. Find temperature rise when its resistance is 124 ohms, and surrounding temperature is 15° C.
  - b) Find the equivalent resistance between A and B for the network shown in figure below.



c) Find current from the source in the following circuit diagram.



2. a) Find the current in 5-ohm resistor in the network shown below by using superposition theorem.



b) Find the branch currents in the circuit of figure below by using nodal analysis.



[8]

[4]

[6]

[6]

[8]

3. a) Find the value of Resistance 'R' such that the load resistance 'R<sub>L</sub>' which is equal to  $4 \Omega$ , will deliver maximum power. Also find that maximum power.



- b) Derive an equation for inductance L in terms of flux linkages and current change.
- c) Calculate the (i) average value and (ii) RMS value of voltage wave shown in figure below:



4. a) Determine the value of current I<sub>1</sub>, I<sub>2</sub> and I and overall factor of the circuit shown in figure below for series and parallel circuit. Also draw the phasor diagram and find the total power consumed by the circuit.



- b) A coil is connected in series with a non-inductive resistance of 30Ω across 240V, 50Hz, 1-φ supply. The reading of voltmeters across the coil is 180 V and across the resistance is 130 V. Calculate,
  - i) Inductance of coil
  - ii) Resistance of coil
  - iii) Power absorbed by coil
  - iv) Power absorbed by whole circuit

5. a) Define power factor and explain why in general it should be kept on high as possible in power supply system.

b) Three similar coils each of resistance  $7\Omega$  and inductance of 0.03 H are connected in Delta to a 400 V, 3 phase, 50 Hz supply. Calculate the line current and the total power consumed.

12

[8]

[8]

[8]

[8]

[8]

[4]

Regular TRIBHUVAN UNIVERSITY Exam. 25 **Full Marks** 80 BE INSTITUTE OF ENGINEERING Level BEL, BEX, BCT, **Examination Control Division** Pass Marks 32 Programme BAME, BIE, B.Agri. 3 hrs. Time

2072 Chaitra

### Subject: - Basic Electrical Engineering (EE401)

Year / Part

I/I

- Candidates are required to give their answers in their own words as far as practicable. V
- Attempt All questions. 1
- The figures in the margin indicate Full Marks. V
- Assume suitable data if necessary.  $\checkmark$
- 1. a) A 60 W, 240 V incandescent filament lamp is switched on at 20°C. The operating temperature of the filament is 2000°C. Determine the current taken by the lamp at the instant of switching ON. the temperature coefficient of resistance of the filament material is 0.0045/K.
  - b) A battery of unknown emf is connected across resistances, as shown in figure below. The voltage drops across the 8  $\Omega$  resistor is 20 V. What will be the current reading in the ammeter? What is the emf of the battery?



#### c) What do you mean by ideal and practical voltage and current sources?

2. a) Find the power dissipation in 15  $\Omega$  resistor shown in figure below using mesh analysis.



b) Find current on load resistor  $R_L$ , if its resistance is 2  $\Omega$ , using superposition theorem. [6]



c) State and explain Norton's theorem with an appropriate example.

[4]

[5]

[6]

[6]

[5]

3. a) Find the value of R<sub>L</sub> for which the maximum power is transferred in the load resistance R<sub>L</sub>. Also find the maximum power that can be transferred to the load resistance R<sub>L</sub>.



- b) Derive the expression for the inductance of inductor in terms of its physical dimensions.
- c) Calculate the average and rms value of full-wave rectified sine wave as shown below.



- 4. a) A circuit consisting of a resistance of 30  $\Omega$  in series with an inductance of 75 mH is connected in parallel with a circuit consisting of a resistance of 20  $\Omega$  in series with a capacitance of 100  $\mu$ F. If the parallel combination is connected to a 240 V, 50 Hz single phase supply, calculate (i) The current in each branch (ii) The total current and power factor and (iii) Power consumed. Also draw a neat phasor diagram.
  - b) For a series path with a resistance of 8 Ω, capacitor of 120µF and an inductance of 0.1 H, a capacitor 180µF is kept in parallel. Then the combination is fed by 240V, 50Hz, 1-φ supply. Calculate branch currents, total current from supply, power factor of whole circuit, active power and reactive power consumed by the circuit. Also show phasor diagram.
- 5. a) Develop relation between phase voltage and line voltage in  $3-\phi$  star connected system. [4]
  - b) For the circuit shown in figure below, calculate the current through the neutral and the total power consumed in the load.



c) Explain with connection diagram the measurement of 3-\$\$ power using two wattmeters.

\*\*\*

[8]

[8]

[8]

[4]

[4]

[4]

[8]

TRIBHUVAN UNIVERSITY 25 **INSTITUTE OF ENGINEERING Examination Control Division** 2072 Kartik

Exam. New Back (2066 & Later Bate					
Level	BE	Full Marks	80		
Programme	BEL, BEX, BCT, BIE, B.Agri.	Pass Marks	32		
Year / Part	I/I	Time	3 hrs.		

Subject: - Basic Electrical Engineering (EE401)

Candidates are required to give their answers in their own words as far as practicable.

- Attempt <u>All</u> questions.
- The figures in the margin indicate Full Marks.

Assume suitable data if necessary.

1. a) Explain ideal current and voltage sources.

[4]

[8]

[8]

[4]

- b) Define temperature coefficient of resistance. The resistance of a certain length of wire is 4.6 $\Omega$  at 20°C and 5.88 $\Omega$  at 80°C. Determine (a) The temperature coefficient of resistance of the wire at 0° (b) The resistance of the wire at 60°C. [8] [4]
- c) State and explain Superposition theorem with an appropriate example.
- 2. a) Find out the current through 5 ohm resistor connected across the terminal c and d in the network shown below using the Venin's theorem.



b) Use Nodal Analysis Method to determine the  $V_a$ ,  $V_b$  and  $V_c$  and calculate current through 2.5  $\Omega$ .



3. a) Find the resistance between the terminals A and B in the circuit segment below.



b) Three capacitors A, B and C have capacitances 10, 50 and 25  $\mu F$  respectively. Calculate:

[6]

[6]

[6]

[6]

[4]

[4]

[8]

[4]

- i) Charge on each when connected in parallel to a 250 V supply
- ii) Total capacitance and
- iii) p.d. across each when connected in series
- c) State Maximum Power Transfer Theorem and also prove "maximum power will be dissipated when R<sub>Internal</sub> = R<sub>L</sub>"
- 4. a) Derive the expression for electrical current in a pure inductive circuit when input power is V<sub>m</sub>Sinwt. Draw the wave form of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power.
  - b) In the given circuit, find the current through the inductor, what is the equivalent impedance?



c) Find the peak factor and form factor of the triangular wave shown in figure below.



- 5. a) Explain the importance of power factor in an ac circuit, with suitable example. How power factor can be improved?
  - b) A three phase star connected system with line voltage 400 V is connected to three loads: 25∠0°, 11∠-20° and 15∠10° (also connected in star). Find the line to line current, total power and current in the neutral of the system.
  - c) Define phase sequence and explain its significance in three phase system.

\*\*\*

	TRIBHUVAN UNI	VERSITY
INSTIT	UTE OF ENG	INEERING
Examina	tion Contr	ol Division
	2071 Shawa	, 18.19

Exam.	New Back (2066	& Later Bat	ch)
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agri.	Pass Marks	32
Year / Part	1/1	Time	3 hrs.

## Subject: - Basic Electrical Engineering (EE401)

- ✓ Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any <u>Five</u> questions.
- ✓ <u>All</u> questions carry equal marks.
- ✓ Assume suitable data if necessary.

1. a) What is the difference between the potential difference and electromotive force?

b) Find I<sub>1</sub>, I<sub>2</sub> and I<sub>3</sub> in the circuit shown in the figure using Kirchh-off's law.



c) What is the value of the unknown resistor 'R' in figure below, if the voltage drop across  $500\Omega$  resistor is 2.5 volts?



2. a) Use the node voltage method (nodal) to find the current flowing through  $10\Omega$  resistor in the network shown figure below.



[6]

[8]

[4]

[6]

b) For the circuit shown in figure below, calculate the current in the 10 ohn using Thevenin's theorem.



3. a) Determine power dissipated in  $3\Omega$  resitor in the circuit shown in figure below using Norton's theorem.



- b) An inductor is to be made with copper wire wound on a circular iron core having mean length of 40 cm with cross-sectional area of 50 sq mm. If the required value of inductance is 500 mH, calculate the number of turns required given that relative permeability of the core is 1500.
- 4. a) A 415 V, 3 phase, 50 HZ induction motor takes 50 KW power from supply mains at 0.72 power factor lagging. A bank of capacitors is connected in delta across the line to improve the overall power factor. Calculate the capacitance per phase in order to raise the power factor to 0.9 lagging.
  - b) Three loads  $(31+j59) \Omega$ ,  $(30-j40)\Omega$  and  $(80+j60)\Omega$  are connected in delta to a 3 phase, 200 V supply. Find the phase currents, line currents and total power absabed.
- 5. a) Define cycle, Time period, angular velocity, frequency, average and rms value of an alternating quality.
  - b) A series circuit consists of resistance equal to 4Ω and inductance of 0.01 H. The applied voltage is 283 sin (300t + 90°)V. Calculate the following: [10]
    - i) Power factor
    - ii) Expression for i(t)
    - iii) The power dissiputed in the circuit
    - iv) Voltage drop across each elements
    - v) Draw a phasor diagram

[8]

[8]

[8]

[8]

[6]

#### 25 TRIBHUVAN UNIVERSITY INSTITUTE OF ENGINEERING Examination Control Division

2070 Ashad

Exam.	New Back (2066 & Later Batch)					
Level	BE	Full Marks 80				
Programme	BEL, BEX, BCT, BIE, B. Agri.	Pass Marks	32			
Year / Part	I/1	Time	3 hrs.			

[6]

[4]

[6]

[6]

[6]

[8]

## Subject: - Basic Electrical Engineering (EE401)

- Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt All questions.
- The figures in the margin indicate <u>Full Marks</u>.
- ✓ Assume suitable data if necessary.
- 1. a) What is the factor responsible for the deviation of the practical sources from their ideal behavior? Explain the effect of this factor on the terminal characteristics of the voltage source.
  - b) Write down the steps to calculate Norton's equivalent resistance in the circuit with a suitable example.
  - c) A conductor material has a free electron density of 10<sup>24</sup> electrons per m<sup>3</sup>. When a voltage is applied a constant drift velocity of 1.5×10<sup>-2</sup> m/s is attained by the electrons. If the cross sectional area of the material is 1 cm<sup>2</sup>, calculate the magnitude of the current.
- a) Explain with neat diagram and write the equations for Delta- Star Conversion and for Star-Delta Conversion. [4]
  - b) Find the equivalent resistance across the terminals A and B,  $R_{AB}$ .



- c) "Thevenin's theorem and Norton's theorem are dual of each other". Justify the statement with suitable example.
- 3. a) Use Superposition theorem to find the current  $I_L$  through 2  $\Omega$  resistors in figure below.



Ą

Find the current passing through 10  $\Omega$  resistor using loop current method.



- b) Calculate the inductance that must be connected in parallel with a 100 MH inductor to give a total inductance of 70 mH. Assume no mutual inductance between the two.
- c) Two impedances (3-4j) and (8+6j) are connected in parallel across an ac voltage source. If the total current drawn from the source in 25 A, find the total active power consumed by the impedances.
- 4. a) Find the average value, rms value of the voltage waveform given below.



b) An Industrial load consists of the following:

i) A load of 200 KVA @ 0.8 power factor lagging

ii) A load of 50 KW @ unity power factor

iii) A load of 48 KW @ 0.6 power factor leading

Calculate the total KW, Total KVAR, Total KVA and the overall power factor.

- 5. a) A 100 KW load at 0.8 lagging power factor is being supplied by a 220 V, 50 Hz source. Calculate the reactive power drawn from the source. If a capacitor connected parallel to the load improves its power factor to 0.9. Find the capacitance of the capacitor. Also calculate the current drawn from the source before and after connecting the capacitor.
  - b) With the help of necessary Phasor diagram and circuit diagram, explain the two wattmeter method of Active Power Measurement in Three Phase AC system? What is the variation of wattmeter readings with load Power Factor?



[4]

[4]

18]

[8]

[8]

4

25 TRIBHUVAN UNIVERSITY	Exam.	. R	egular	
INSTITUTE OF ENGINEERING	Level	BE	Full Marks	80
<b>Examination Control Division</b>	Programme	BEL,BEX,BCT,BIE, B.Agri.	Pass Marks	32 ·
2070 Chaitra	Year / Part	I/I	Time	3 hrs.

#### Subject: - Basic Electrical Engineering (EE401)

✓ Candidates are required to give their answers in their own words as far as practicable.

✓ Attempt <u>All</u> questions.

The figures in the margin indicate <u>Full Marks</u>.

✓ Assume suitable data if necessary.

- 1. a) What do you understand by terms 'resistance' and 'resistivity'? On what factors the resistance offered by a conductor depends?
  - b) Two resistors made of different materials having temperature coefficients of resistance  $\alpha_1 = 0.004/^{\circ}$ C and  $\alpha_2 = 0.005/C^{\circ}$  are connected in parallel and consume equal power at 15°C. What is the rate of power consumed in resistance R<sub>2</sub> to that in R<sub>1</sub> at 70 c<sup>o</sup>?
  - c) Calculate the value of unknown resistance R in the circuit shown below and the current flowing through it when the current in the branch OC is zero.



2. a) Calculate the output voltage, V<sub>o</sub> for the circuit shown in figure below using Kirchoff's laws.



b) Determine the power dissipated by  $5\Omega$  resistor in the circuit shown in figure below by applying nodal voltage analysis.



c) State and explain superposition Theorem with an appropriate example.

[5]

[4]

[6]

[6]



[5]

3. a) For the circuit shown in figure below, what will be the value of R<sub>L</sub> to get the maximum power? What is the maximum power delivered to the load?



b) Determine the current in  $20\Omega$  resistor of the network shown in figure below using Star Delta Transformation



- c) State the definition of the capacitance and from it write an equation for the charge stored in a capacitor.
- 4. a) Derive the equation for instantaneous current flowing through a pure capacitor when excited by AC sinusoidal voltage  $V = V_m$  Sinot. Draw the waveform of voltage and current and phasor diagram of the circuit. Show analytically and graphically that it does not consume real power.
  - b) A coil takes 1.3 kVA nd 1.2 kVAR when connected to a 240 V, 50 Hz sinusoidal supply. Calculate: (i) Power dissipated (ii) Current and (c) Inductance of the coil.
  - c) A Circuit consisting of a resistance of  $30\Omega$  in series with an inductance of 75mH is connected in parallel with a circuit consisting of a resistance of  $20\Omega$  in series with a capacitance of  $100\mu$ F, if the parallel combination is connected to a 240V, 50Hz, single-phase supply. Calculate (i) The total current (ii) Power factor (iii) Active and reactive power. Also draw a neat phasor diagram.
- 5. a) What are the two ways of connecting a 3-phase system? Draw their phasor diagrams and write down the relationship between phase and line voltages and phase and line current for these system.
  - b) A 220 V, 3-phase voltage is applied to a balanced delta connected 3-phase load of phase impedance (15+i20)Ω. Calculate:
    - i) The phase voltages
    - ii) The phasor current in each line
    - iii) The power consumed per phase
    - iv) Draw the phasor diagram
    - v) What is the phasor sum of three line currents? Why does it have this value?
  - c) Explain 2-wattmeter method for the measurement of power in a balanced three phase load.

[8]

[4]



[4]

[4]

[4]

[8]

[8]

[4]

#### 25 TRIBHUVAN UNIVERSITY INSTITUTE OF ENGINEERING

**Examination Control Division** 

#### 2069 Chaitra

Exam.	R	legular	
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agri.	Pass Marks	32
Year / Part	I/I	Time	3 hrs.

[4]

[4]

[8]

[1

ſ

#### **Subject**: - Basic Electrical Engineering (EE401)

- $\checkmark$  Candidates are required to give their answers in their own words as far as practicable.
- ✓ Attempt any <u>Five</u> questions.
- ✓ The figures in the margin indicate *Full Marks*.
- ✓ Assume suitable data if necessary.
- ✓T. \*a) Explain the methods for converting practical current source in to practical voltage source.
  - b) Calculate the power which would be dissipated in a 75  $\Omega$  resistor connected across XY in the network shown below.



Find the currents I<sub>1</sub>, I<sub>2</sub>, I<sub>3</sub> using Kirchhoff's Law and also find the power output of each voltage source of figure below?





- (2. +a) The resistivity of a metal alloy is  $50 \times 10^{-8} \Omega$ -m. A sheet of material 15 cm long, 6 cm wide and 0.014 cm thick. Calculate the resistance in the direction: (a) along the length and (b) along the thickness.
  - b) Use Norton's theorem to calculate the value of R that will absorb maximum power from the circuit shown in the figure below. Also calculate the maximum power drawn by it.





In the network shown below, find the value of resistance R and the current through it c) when the current through branch DA is zero.



3. (a) Find the current through the 10  $\Omega$  resistor using loop-current method?



Fig: 3.1



b) Find the current I in the circuit of figure below by applying nodal voltage method.



a) Explain generation of sinusoidal emf with diagram and define angular velocity.

- b) A sinusoidal voltage is applied to three parallel branches yielding branch currents,  $i_1=14.14$  Sin( $\omega t$ -45°),  $i_2=28.3$  Cos( $\omega t$ -60°) and  $i_3=7.07$  Sin( $\omega t$ +60°) (i) Find the complete time expression for the source current (ii) Draw the phasor diagram in terms of effective values. Use the voltage as reference.
- c) Define inductance and derive relation for connection of inductors connected in parallel connection.

[6]

[8]

[6]

[4]



[4]

- 5. a) For the parallel circuit shown below, calculate:
  - (i) RMS value for current, power factors and active power of path 1.
  - (ii) RMS value of current, power factor and reactive power of path 2.
  - (iii) RMS value of current and power factor of the whole circuit.



- b) A three phase induction motor takes 50KW at 415V, 50Hz and a power factor of 0.72 lagging. Determine the KVAR rating of capacitor bank to improve the power factor to 0.9 lagging. What capacitance per phase is required if the capacitor bank is connected in star connection? What is the advantage of power factor correction from the source point of view and from the point of view of motor itself?
- 6. a) In the network shown in figure below, determine:
  - i) Total impedance
  - ii) Total current
  - iii) The current in each branch
  - iv) The overall power factor
  - v) Volt amperes, Active Power and Reactive Power





\_b) In a 3-phase, 4 wire Wye connected system the phase voltage  $V_{ph} = 200V$ , and its frequency is 60Hz. The load impedance components are  $R_1 = 100\Omega$ ,  $R_2 = 100\Omega$ ,  $C_2 = 66.3 \ \mu\text{F}$ ,  $R_3 = 100\Omega$ ,  $L_3 = 159.2\text{mH}$ . Calculate the three line currents and the neutral current.

[8]

[8]

[8]

INSTITUTE CONSCRIPCING     Level     EE     Harvaris     ot       Examination Control Division     Programme     BEL, BEX, BCT, BIE, B.Agri     Pass Marks     32       2068 Baishakh     Year / Part     1/1     Time     3 hrs.	- 25 TRIBHUVAN UNIVERSITY	Exam.	Pagu	lør / Back	
Examination Control DivisionProgrammeBEL, BEX, BCT, BIE, B.AgriPass Marks322068 BaishakhYear / Part1/1Time3 hrs.	INSTITUTE WE ENGLADERING	J L.vel	ÉE -	S. TEMATAS	υ
2068 Baishakh Year / Part 1/1 Time 3 hrs.	Examination Control Divis	sion Programme	BEL, BEX, BCT, BIE, B.Agri	Pass Marks	. 32
	2068 Baishakh	Year / Part	I/I	Time	3 hrs.

#### Subject: - Basic Electrical Engineering

Candidates are required to give their answers in their own words as far as practicable.

Attempt any *Five* questions.

The figures in the margin indicate **Full Marks**.

Assume suitable data if necessary.

a) The temperature rise of a m/c field winding was determined by the measurement of the winding resistance. At 20°C the field resistance was 150Ω. After running the m/c for 6 hours at full load, the resistance was 175Ω. The temperature coefficient of resistance of the copper winding is 4.3 × 10<sup>-3</sup>/k at °C. Determine the temperature rise of the m/c.

b) Find I<sub>1</sub>, I<sub>2</sub>, and I<sub>3</sub>, in the circuit shown in the figure using Kirchhoff's law.



2. a) Use Superposition theorem to find the current flowing through the  $10\Omega$  resistor shown in the figure.



- b) State Thevenin's theorem and give the procedure for Thevenizing a circuit. Explain the major advantages offered by use of this theorem.
- 3. a) Use the node voltage method (Nodal) to find the current flowing through  $10\Omega$  resistor in the network shown below.



[6] [10]

[8]

[8]

[8]

b) Determine the power dissipated in  $3\Omega$  resistor in the circuit shown below using Norton's theorem.



- a) An rms voltage of  $100 \angle 0^\circ$  is applied to the series combination of  $\overline{Z}_1$  and  $\overline{Z}_2$  where  $\overline{Z}_1 = 20 \angle 30^\circ$ . The effective voltage drop across  $\overline{Z}_2$  is known to be  $40 \angle -30^\circ V$ . Find the reactive component of  $\overline{Z}_2$ .
- b) For the parallel circuit shown below, calculate:
  - i) RMS value of current, power factor, active and reactive power of path 1
  - ii) RMS value of current, power factor, active and reactive power of path 2
  - iii) RMS value of current, power factor, active and reactive power of the whole circuit



- 5. a) Define cycle, Time period, angular velocity, frequency, average and rms value of an alternating quantity.
  - b) A series circuit consists of resistance equal to 4Ω and inductance of 0.01H. The applied voltage is 283 sin (300t + 90°)V. Calculate the followings: [10]
    - i) Power factor
    - ii) Expression for i(t)
    - iii) The power dissipated in the circuit
    - iv) Voltage drop across each elements and
    - v) Draw a phasor diagram
- 6. a) A 415V, 3 phase, 50Hz induction motor takes 50kW power from supply mains at 0.72 power factor lagging. Capacitors are connected in delta across the line to improve the overall power factor. Calculate the capacitance per phase in order to raise the power factor to 0.9 lagging.
  - b) Three loads  $(31 + j59)\Omega$ ,  $(30 j40)\Omega$  and  $(80 + j60)\Omega$  are connected in delta to a 3 phase, 200V supply. Find the phase currents, line currents and total power absorbed.

[6]

121

[8] [8]

TRIBHUVAN UNIVERSITY	Exam.		NUTRE ST	
INSTITUTE OF ENGINEERING	Level	BE	Full Marks	80
Examination Control Division	Programme	BEL, BEX, BCT, BIE, B. Agri.	Pass Marks	32
2068 Chaitra	Year / Part	1/1	Time	3 hrs.

#### Subject: - Basic Electrical Engineering (EE 401)

Candidates are required to give their answers in their own words as far as practicable. Attempt any Five questions.

The figures in the margin indicate Full Marks.

Assume suitable data if necessary.

- a) Explain emf, potential difference and current with a circuit diagram.
- b) The temperature rise of the machine field winding was determined by the measurement of the winding resistance at 20°C the field winding resistance was 160 Ohm(Ω). After running the machine for some hours at full load the resistance is 185 Ω. If the temperature coefficient of resistance of the copper winding is 4.3 × 10<sup>-6</sup>/°C at 0°C. Determine the temperature rise of the machine.
- c) Find the equivalent resistance in the figure shown, and power dissipated in the  $5\Omega$  resistor.



2. a) Calculate the value of R that will absorb maximum power from the circuit (shown in the figure). Also calculate the maximum power drawn by it.



b) State Norton's description theorem and list the steps for Nortonizing a circuit. Compare the Norton's equivalent circuit to the Thevenin's equivalent circuit.

c) What is the total cost of using the following at Rs 7 per killowatt hour?

- i) A 1200 W toaster for 30 min
- ii) Six 50 W bulbs for 4 hours

[4]

[6]

[6]

[6]

[6]

[4]

- iii) A 400 W washing machine for 45 min.iv) A 4800 W electric cloths dryer for 20 min.
- 3. a) Use Nodal analysis method to calculate the current through the  $15\Omega$  resistor in the



[8]

[4]

[4]

[6]

[5]

[5]

[8]

[8]

b) Find the current I as shown in figure below using star - delta transformation.



- c) An air cored coil is 2.5cm long and has an average cross-sectional area of  $2cm^2$ . Determine the number of turns if the coil has an inductance of 100  $\mu$ H.
- 4. a) Calculate the average value, rms value, form factor and peak factor of the saw tooth wave as shown in figure below.



- b) What do you mean by reactive power in AC circuit? Explain it by constructing phasor diagram for real power, reactive power and apparent power.
- c) Describe and illustrate the phasor relationship that exist between the voltage that appears across the terminals of a pure capacitor and the current that flows through it in steady state when the capacitor is excited by a sinusoidal source.
- 5. a) A voltage of 200∠0° V is applied across impedances in parallel. The value of impedances are (12 + j16)Ω and (10-j20)Ω. Determine the KW, KVA and KVAR in each branch and the power factor of the whole circuit.
  - A delta connected load of  $Z_{AB} = 52 \angle 45^{\circ}\Omega$ ,  $Z_{BC} = 52 \angle -30^{\circ}\Omega$  and  $Z_{CA} = 10 \angle 0^{\circ}\Omega$  are connected to a 380V, 3 phase ac source. Find the magnitude of the line currents and total power absored by loads, when phase sequence is ABC.

6(a) A single phase motor takes a current of 40A at pf 0.7 lagging from a 440V, 50HZ supply. What value must a shunting capacitor have to raise the power factor to 0.9 - lagging.

[4]

[6]

b) What are the advantages of three phase AC system over signal phase ac system?

c) Determine current in  $5\Omega$  resistor by mesh analysis in figure below.

[8]

[4]

[4]

[6]

[5]

[5]

[8]

[8]

t

1





#### 25 TRIBHUVAN UNIVERSITY INSTITUTE OF ENGINEERING Examination Control Division

Exam.	Regular/Back		
Level	BE	Full Marks	80
Programme	BEL, BEX, BCT, BIE, B.Agri.	Pass Marks	32
Year / Part	I/I	Time	3 hrs.

#### 2067 Ashadh

#### Subject: - Basic Electrical Engineering

Candidates are required to give their answers in their own words as far as practicable.

✓ Attempt any *Five* questions.

<u>All</u> questions carry equal marks.

✓ Assume suitable data if necessary.

- a) The temperature rise of the machine field winding was determined by the measurement of the winding resistance. At 20°C the field resistance was 150 ohm. After running the m/c for 6 hours at full load, the resistance was found to be 175 ohm. If the temperature coefficients of resistance of the copper winding is 1.57×10<sup>-5</sup>/°C at 0°C, determine the temperature rise of the machine.
  - b) What are ideal and practical voltage and current sources? Explain.
- 2. a) Calculate the current in the  $15\Omega$  resistor in the network shown in figure below using superposition theorem.



b) Determine the current  $I_L$  through 15 $\Omega$  resistor in the network by Norton's theorem.



3. a) Use nodal method to find the current through  $10\Omega$  resistor for circuit shown below.



b) Calculate the value of R to receive maximum power and the maximum power received by it for the circuit shown below.



- 4. a) A series circuit consists of a resistance equal to  $4\Omega$  and inductance of 0.01H. The applied voltage is  $v = 283 \sin (300t + 90^\circ)$  volts. Find
  - i) The power dissipated in the circuit
  - ii) The expression for i(t)
  - iii) Power factor and
  - iv) Draw a phasor diagram
  - b) For the circuit below, calculate
    - i) Magnitude and phase angles of current in each of the branches,
    - ii) Active, reactive and apparent power and power factor of the circuit, and
    - iii) Draw the vector diagram indicating branch currents and supply voltage



- 5. a) Describe the advantages of three phase AC system over single-phase AC system.
  - b) Three phase balanced load consists of three similar coils, each of resistance  $50\Omega$  and inductance of 0.3H. The supply voltage is 415V, 50Hz. Calculate (i) The line current (ii) The power factor (iii) Total power consumed and (iv) Draw the phasor diagram. Take R×B as phase sequence.
- 6. a) Define power factor and explain the disadvantages and causes of low power factor?
  - b) A single-phase 50Hz motor takes 20A at 0.65 power factor lagging from a 230V sinusoidal supply. Calculate the KVar rating and capacitance to be connected in parallel to raise the power factor to 0.9 lagging. What is the new supply current?

